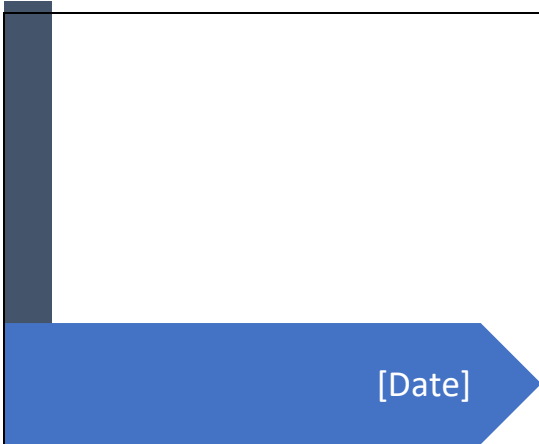
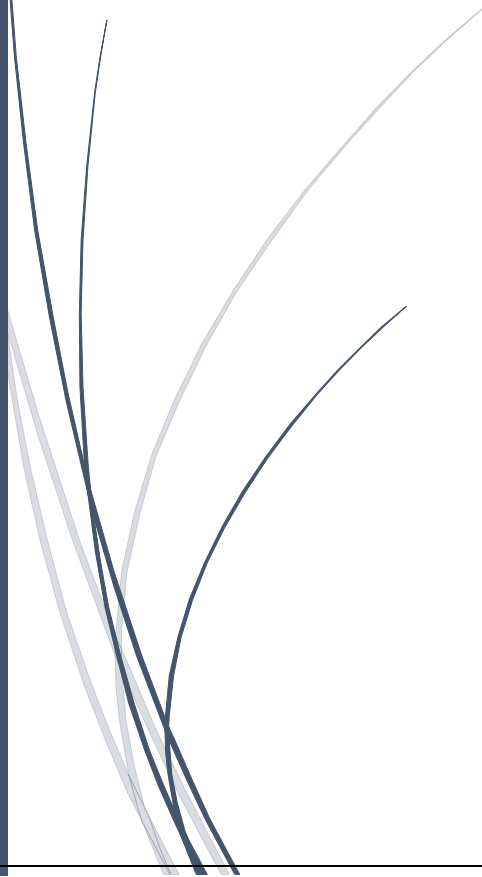


A dark blue vertical bar is on the left. A blue arrow points right from it, containing the text "[Date]".

[Date]

Computer Architecture

Week 13

Several thin, curved lines in shades of blue and grey originate from the left side and sweep upwards and to the right.



Name: Horriya Noor

Sap ID: 64048

Semester: 4th Semester



Department: BSCS


Half Adder:

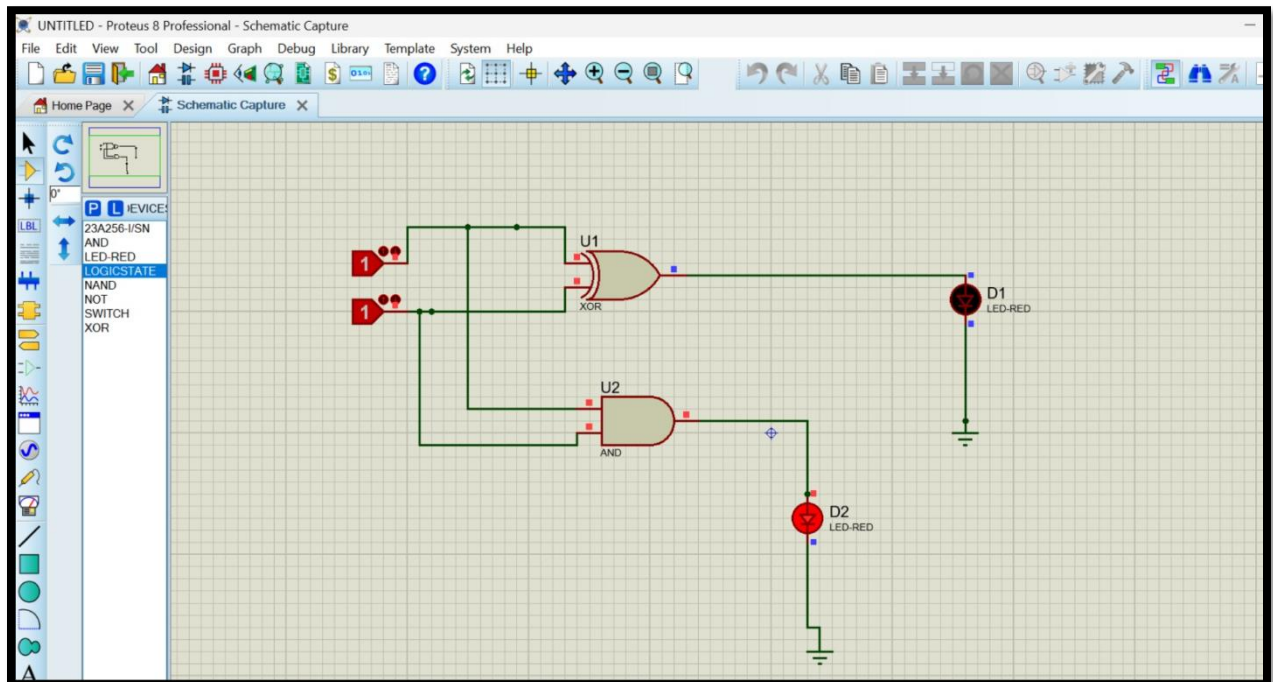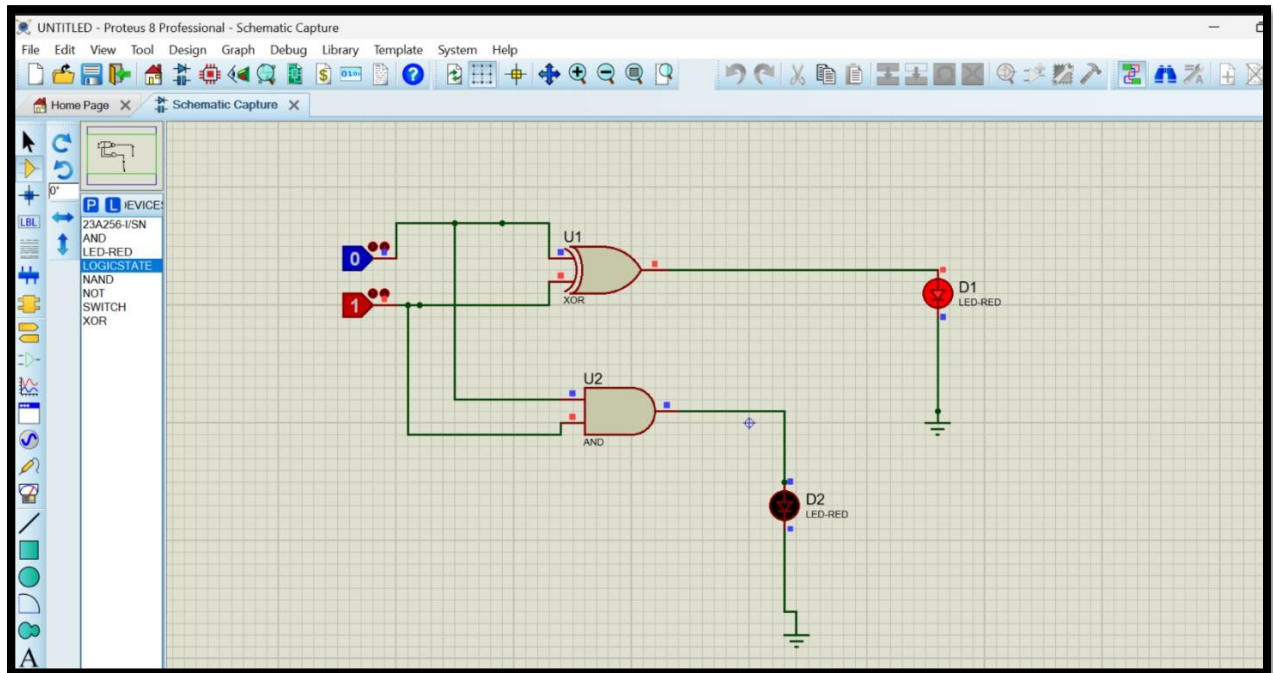

2. Design and simulate a half Subtractor.

HALF SUBTRACTOR:

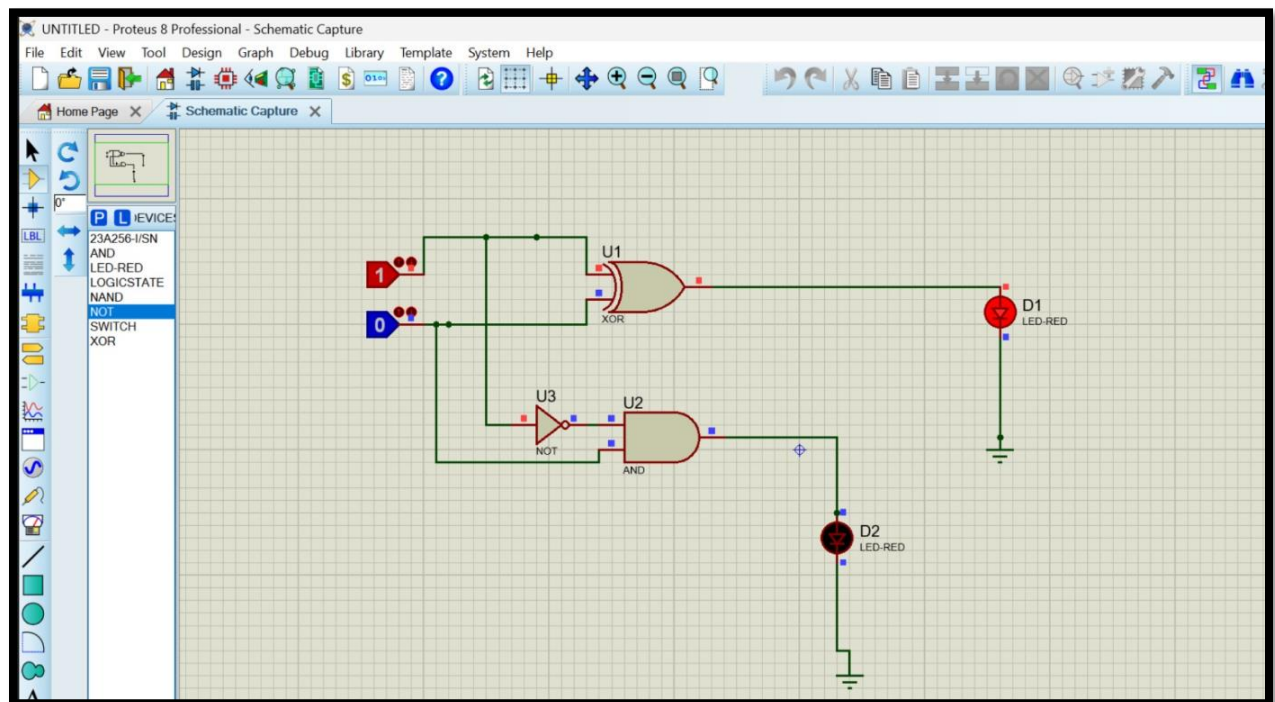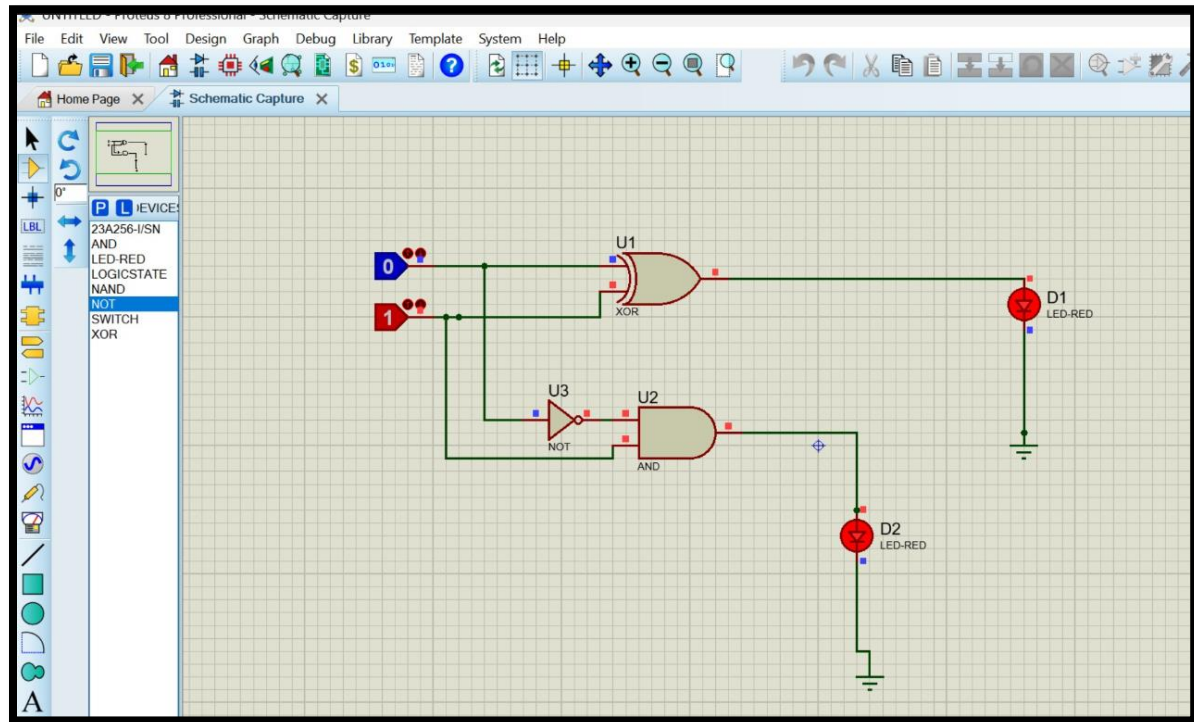

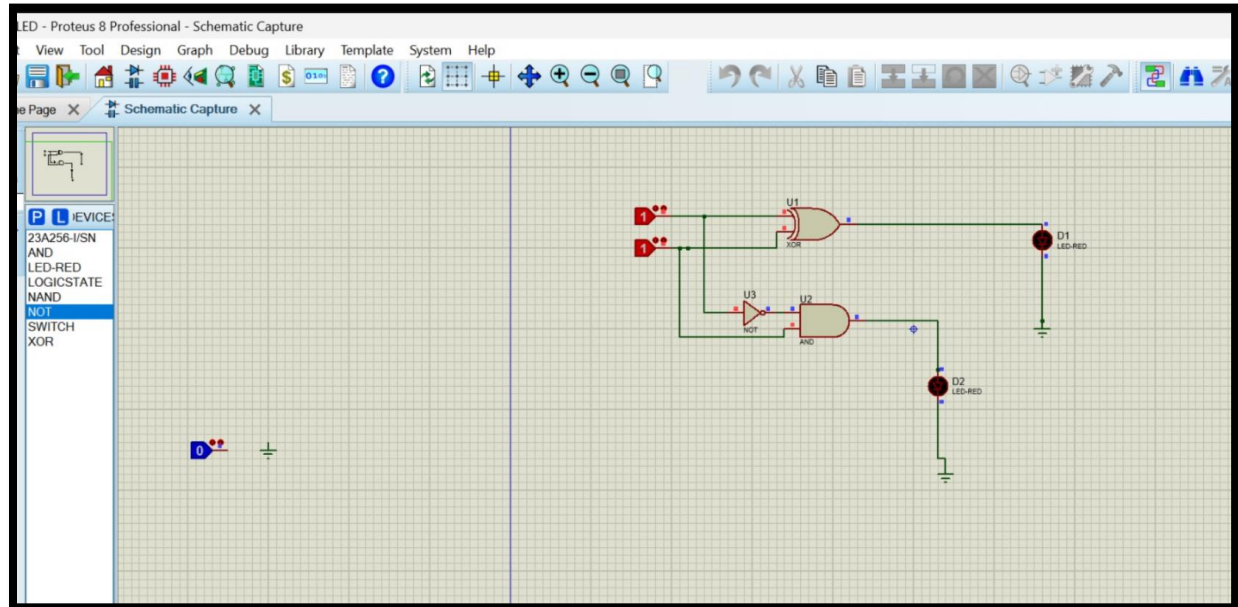

Design and simulate a simple NAND Gate using switches instead of logic states.

NAND GATE:

