



COMPUTER ARCHITECTURE LAB

Week # 12



Name: Horriya Noor

Sap ID: 64048

Semester: 4th


Department: BSCS

Lab Task:


Verify all the basic logic gates using the proteus simulation tool and check the output given in the above table. Take screenshots and prepare a pdf file.

NOT Gate:

OFF State:

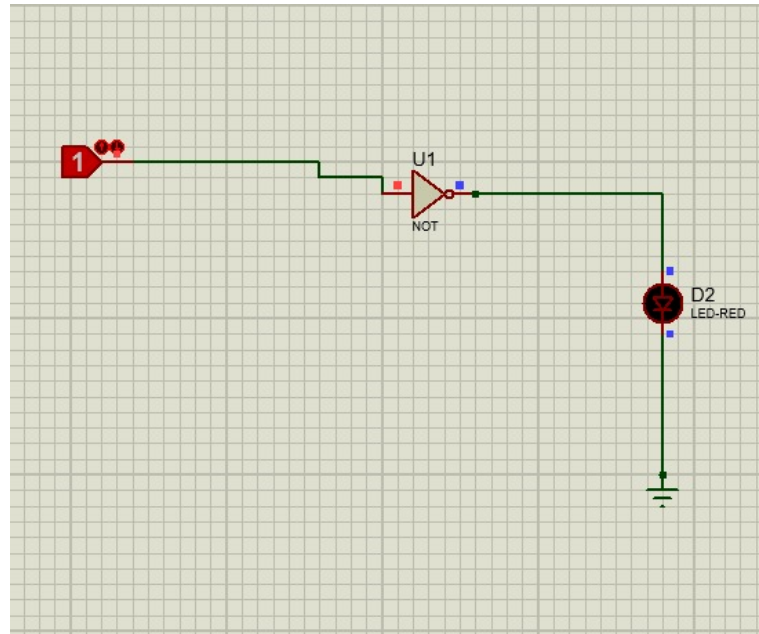


ON State:

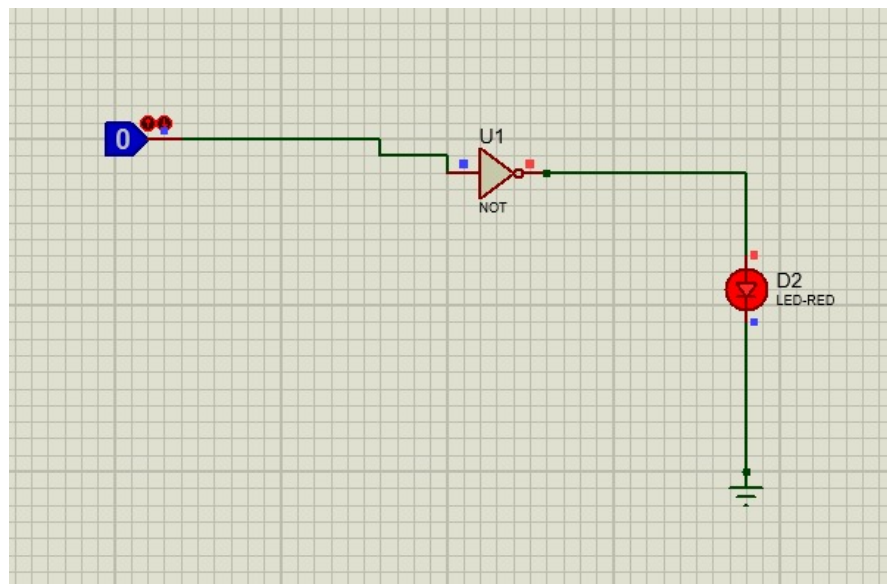


AND Gate:

Off State:

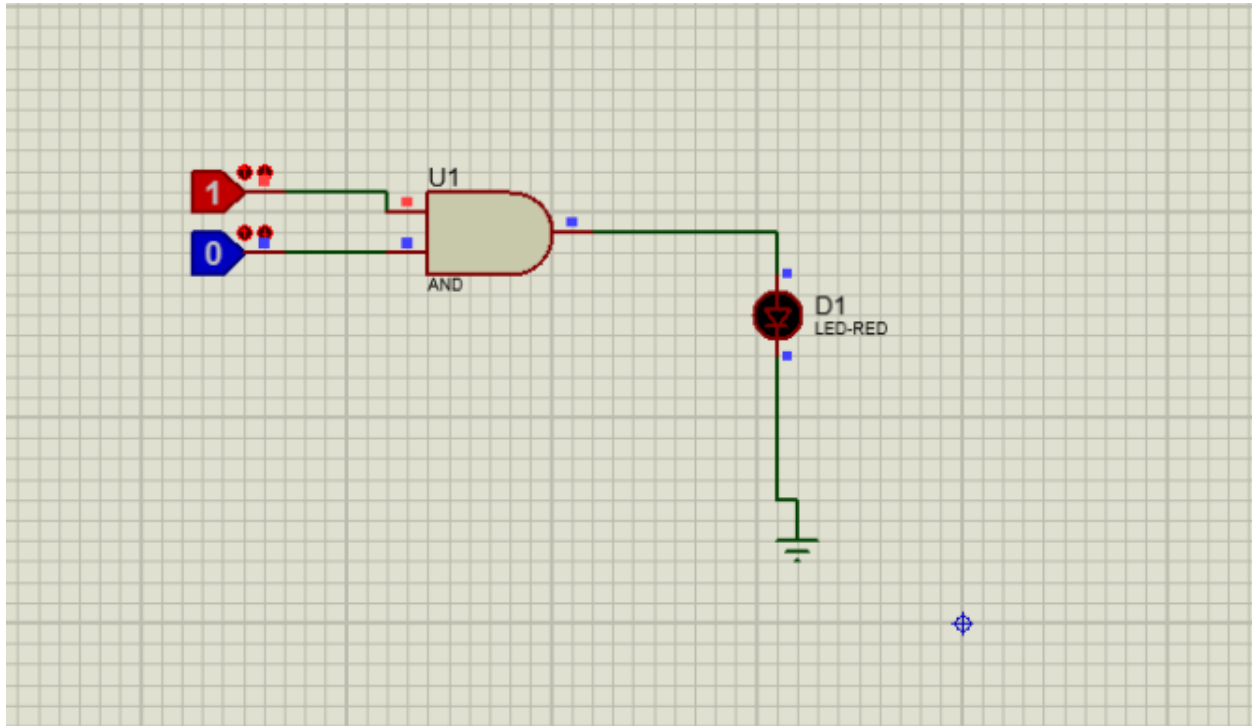


ON State:

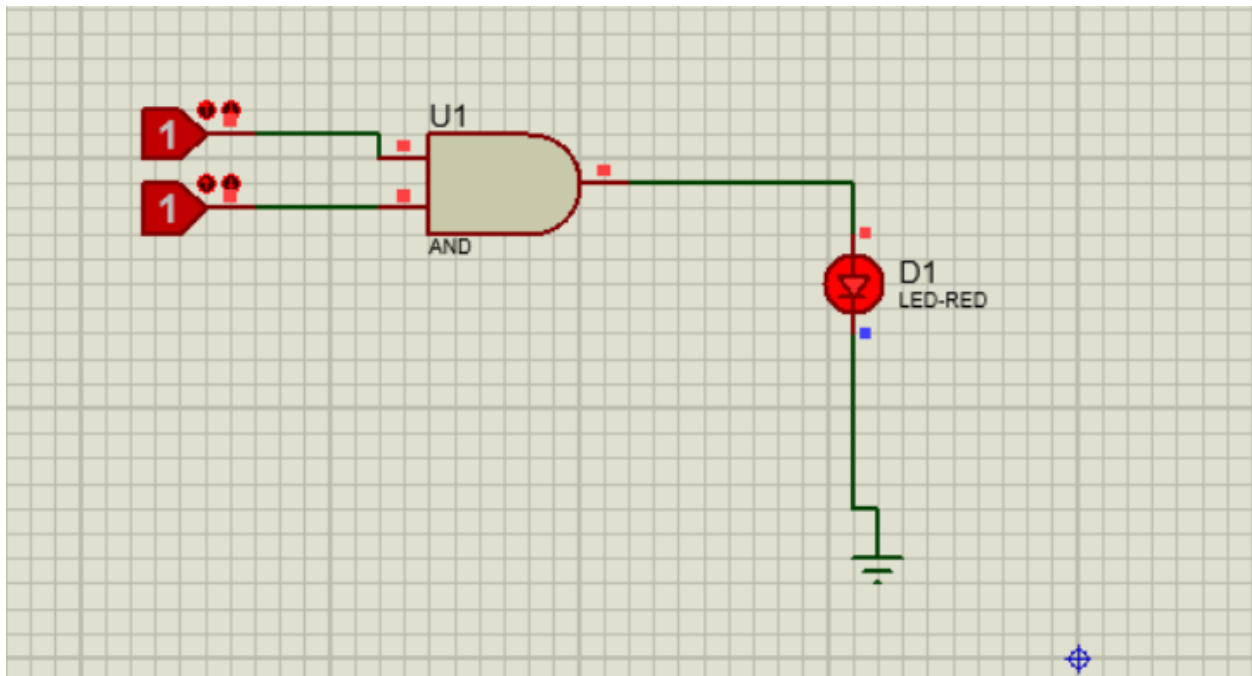


OR Gate:

OFF State:

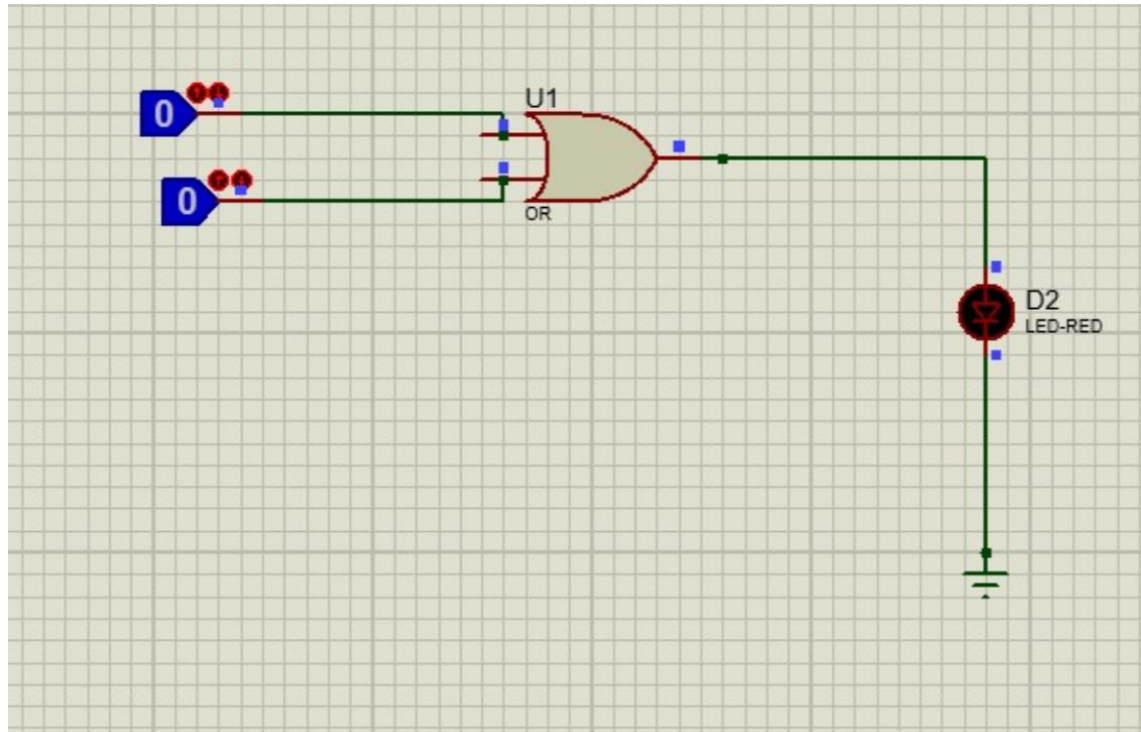


ON State:

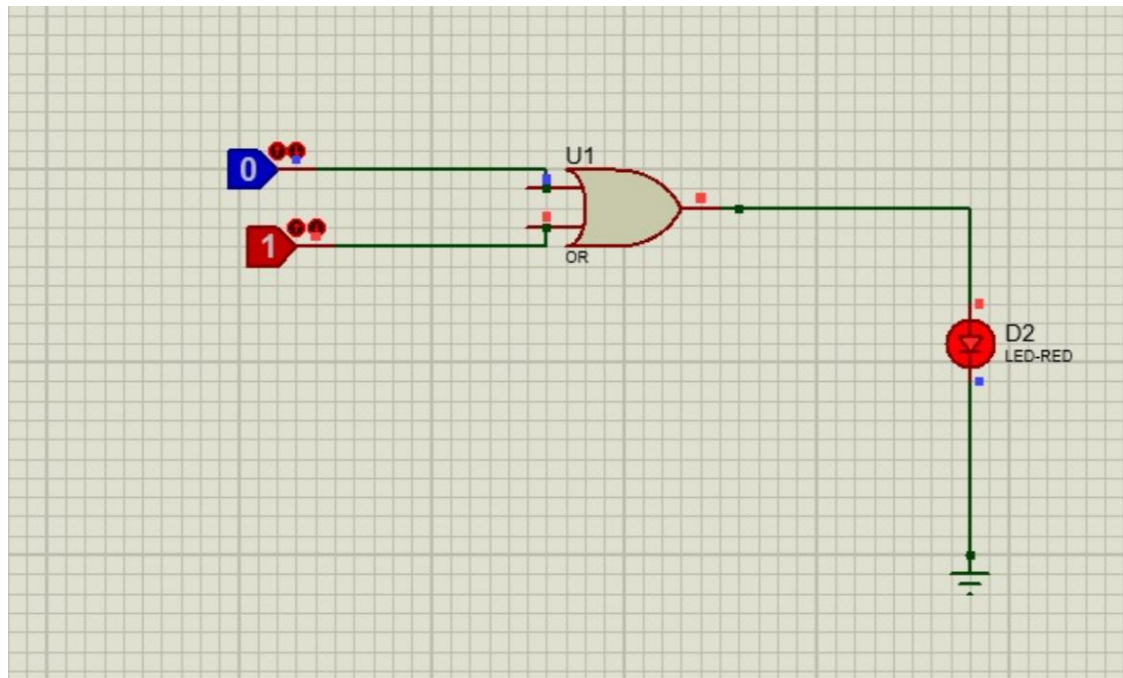


XOR Gate:

OFF State:

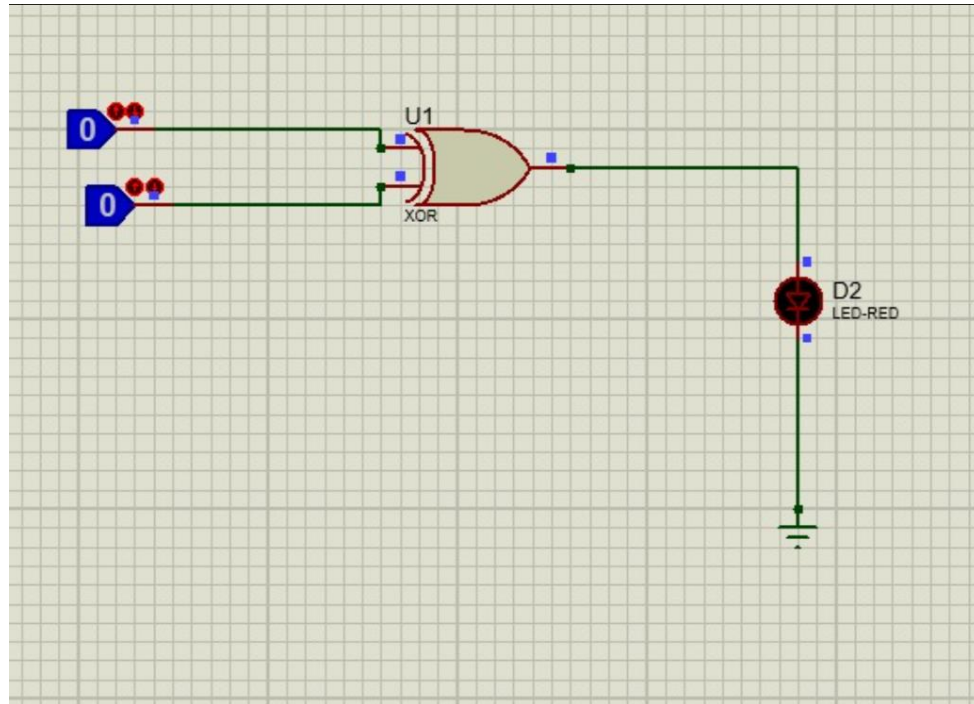


ON State:

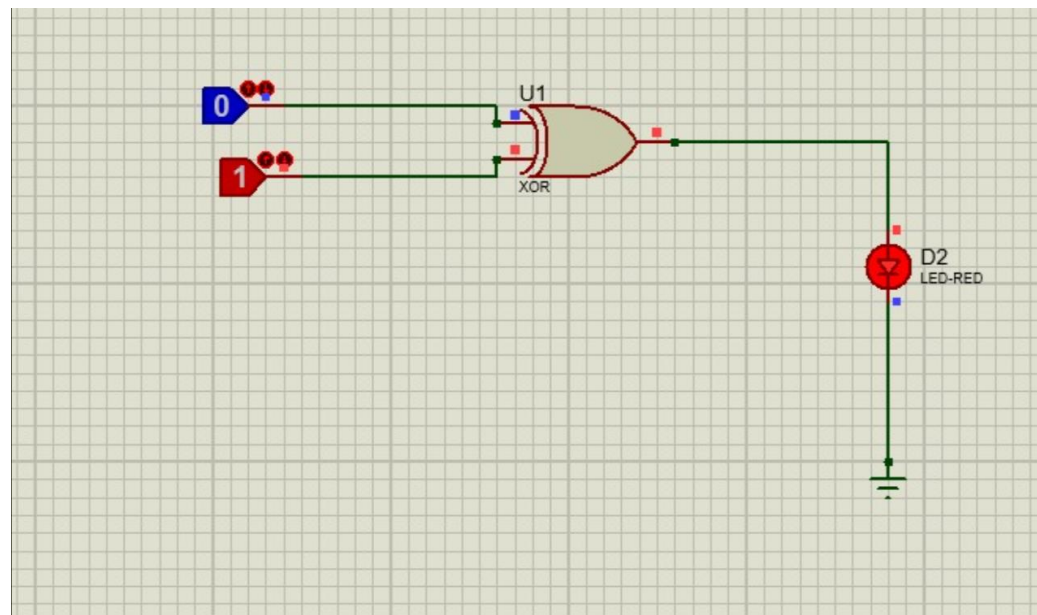


XNOR Gate:

OFF State:

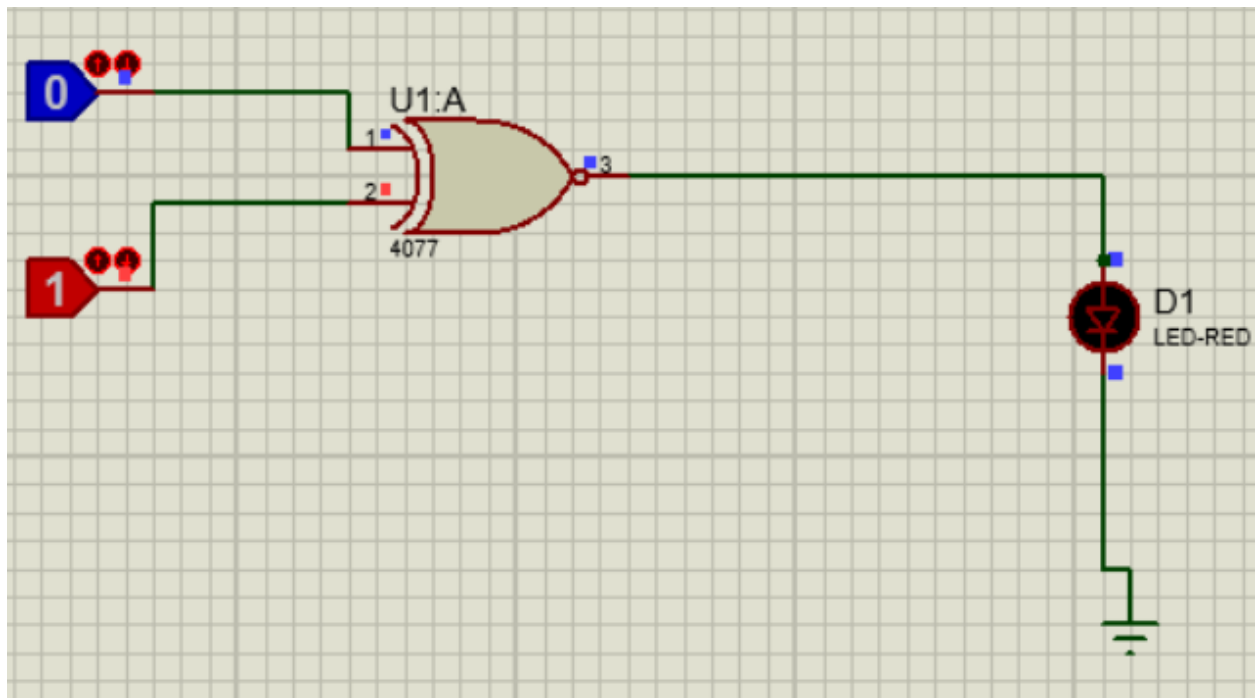


ON State:

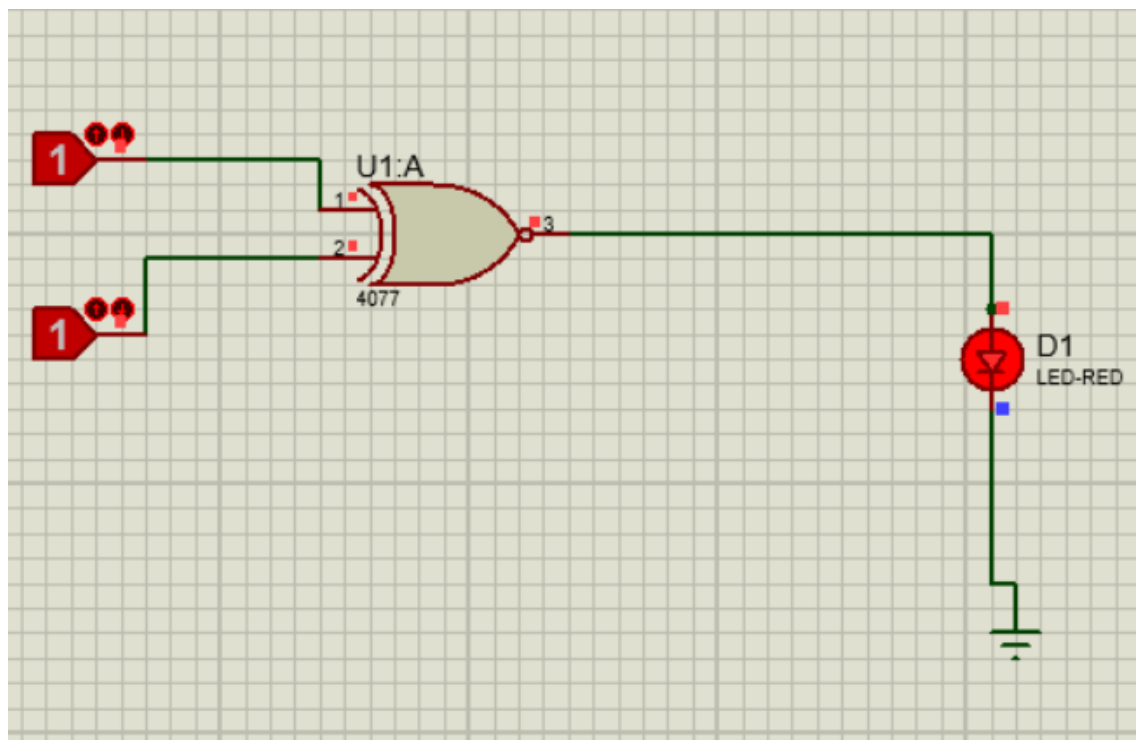


NAND Gate:

OFF State:

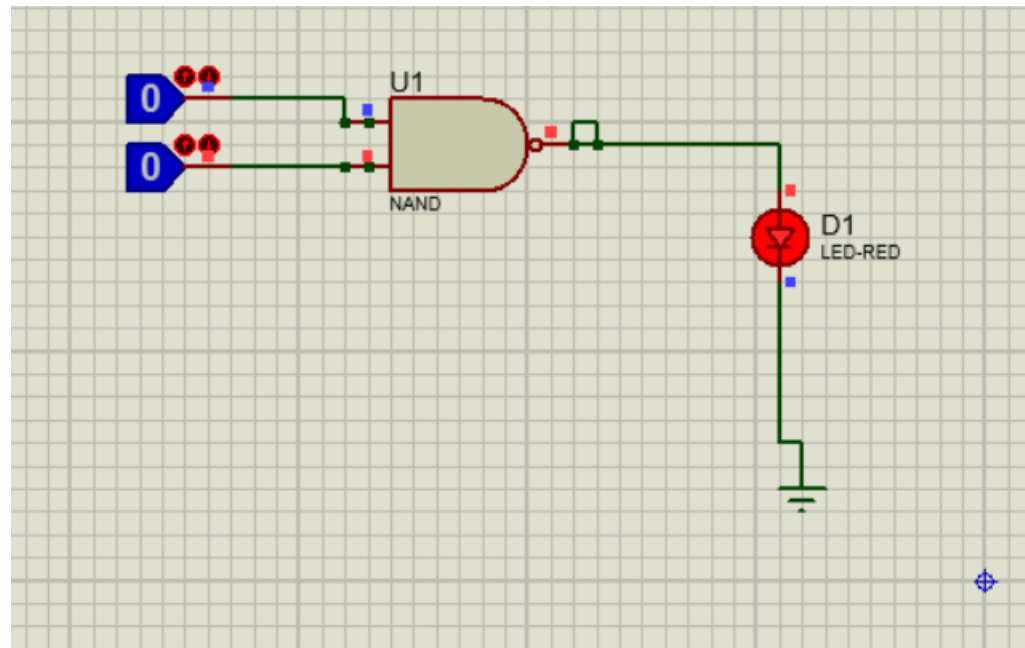


ON State:

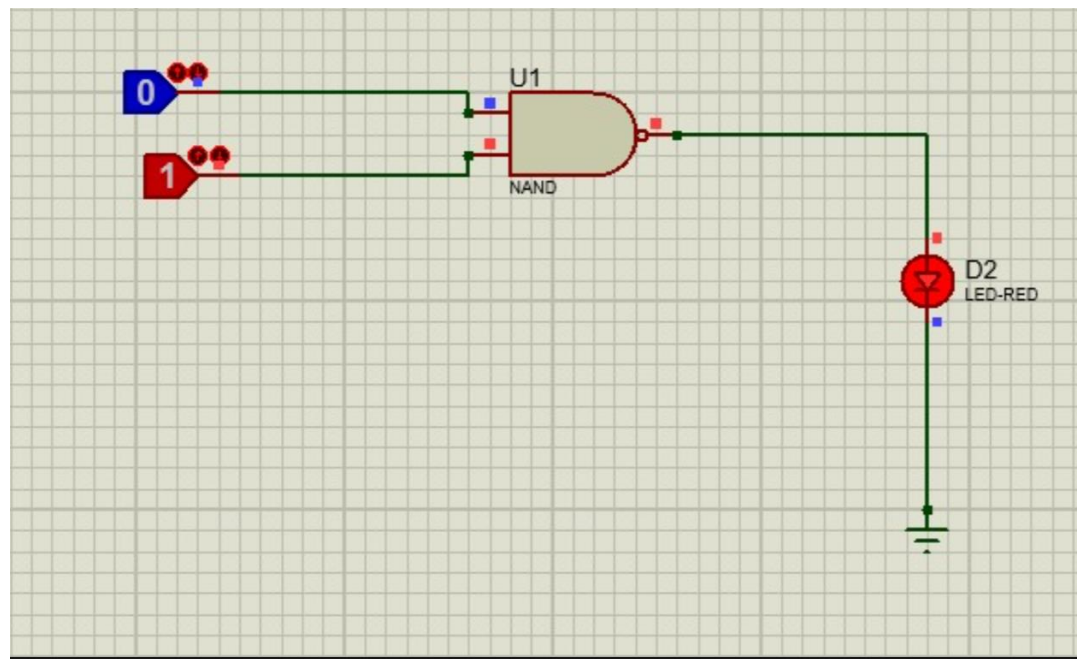

NOR Gate:

OFF State:

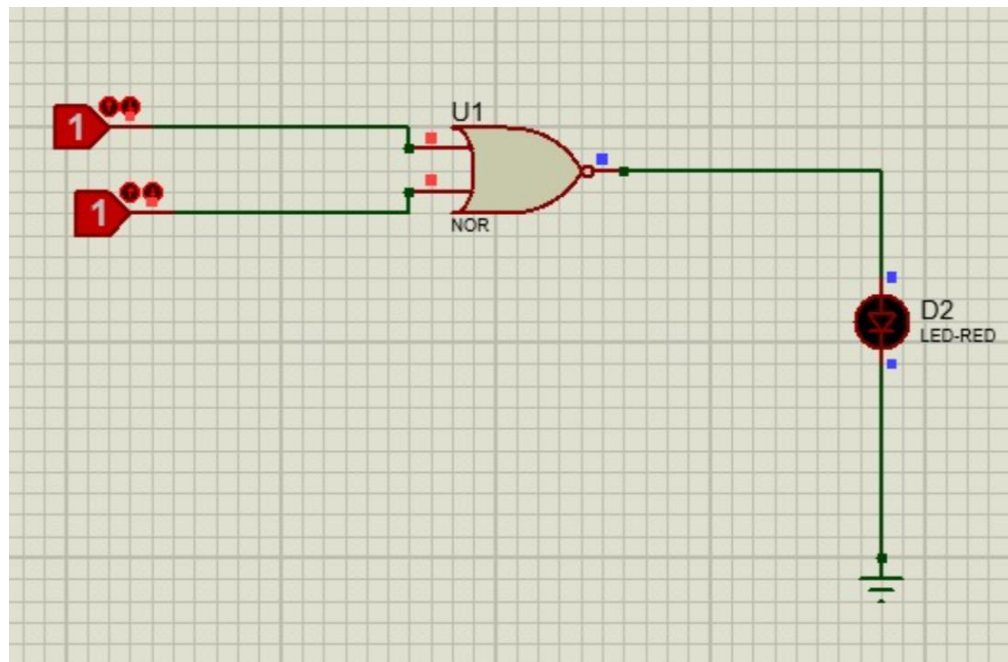

ON State:

